

Counters

MC. Martin González Pérez




CONFIDENTIAL

Agenda


- Counters

CONFIDENTIAL

Addition

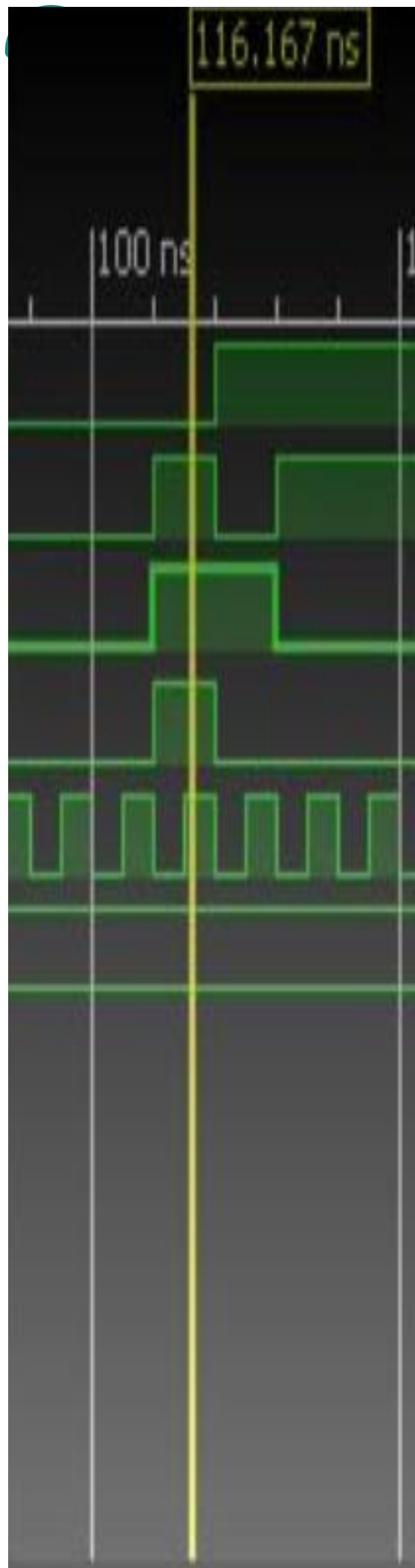

Counter

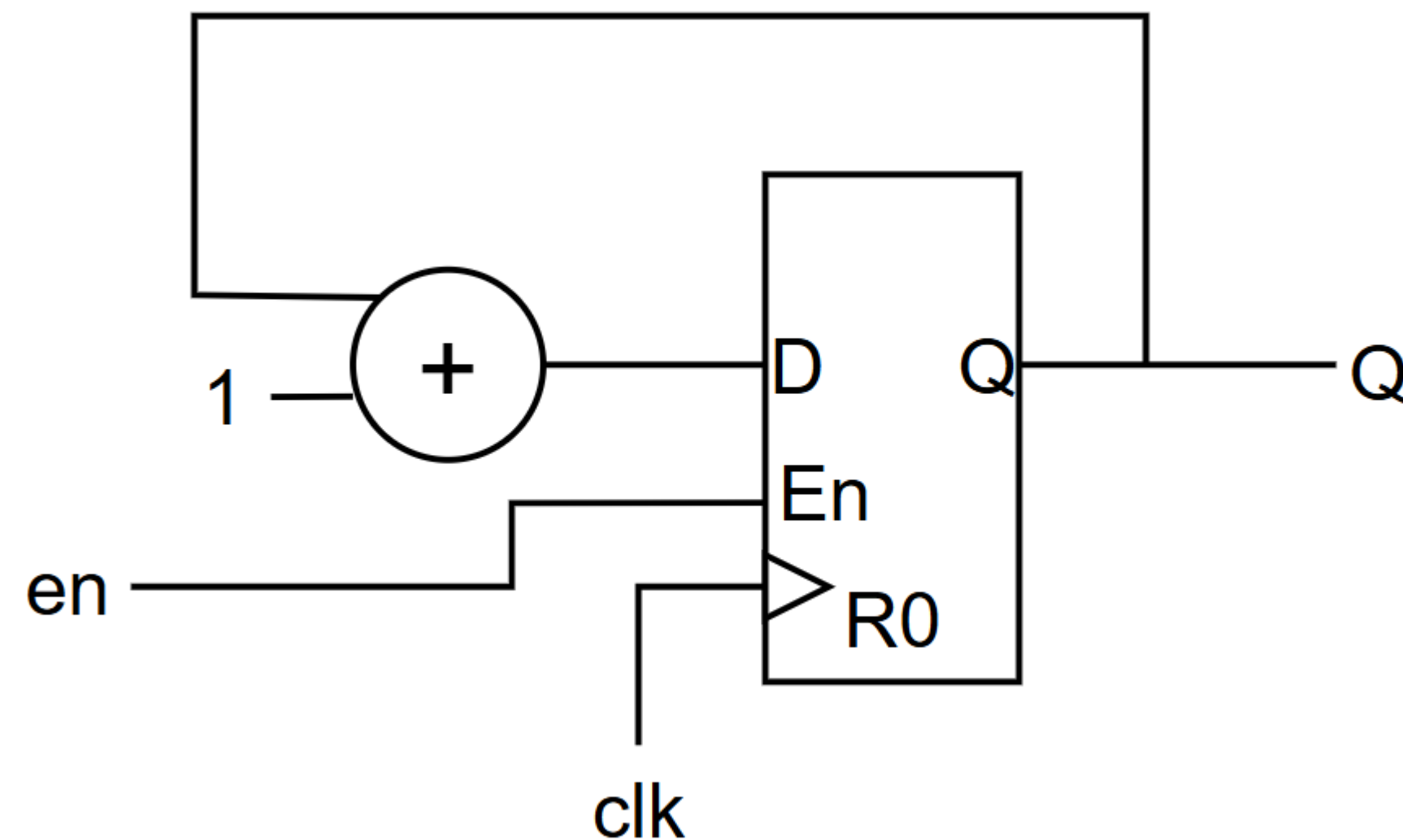


```

if (en)
    Q = Q + 1;
else
    Q = Q;

```

Counter with preset

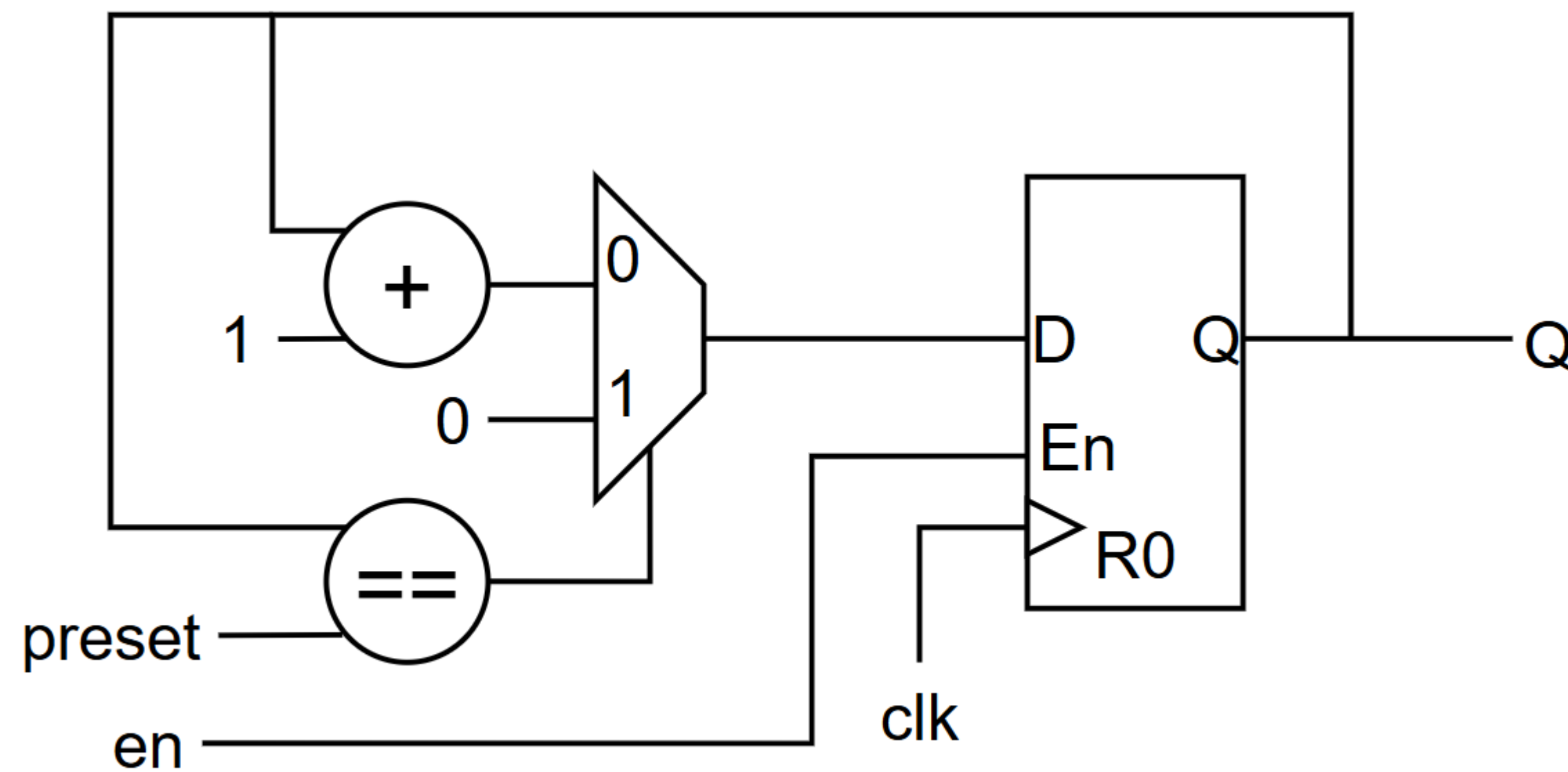

```

if (en) {
    if (Q==preset) {
        Q = 0;
    }
    else
        Q = Q + 1;
}
else
    Q = Q;

```


Others features

Common characteristics of a digital counter

- Counting direction (up, down, bidirectional)
- Configurable range (max value before restarting)
- Load (A specific value can be loaded to the counter)


CONFIDENTIAL

Frequency divider



Frequency divider

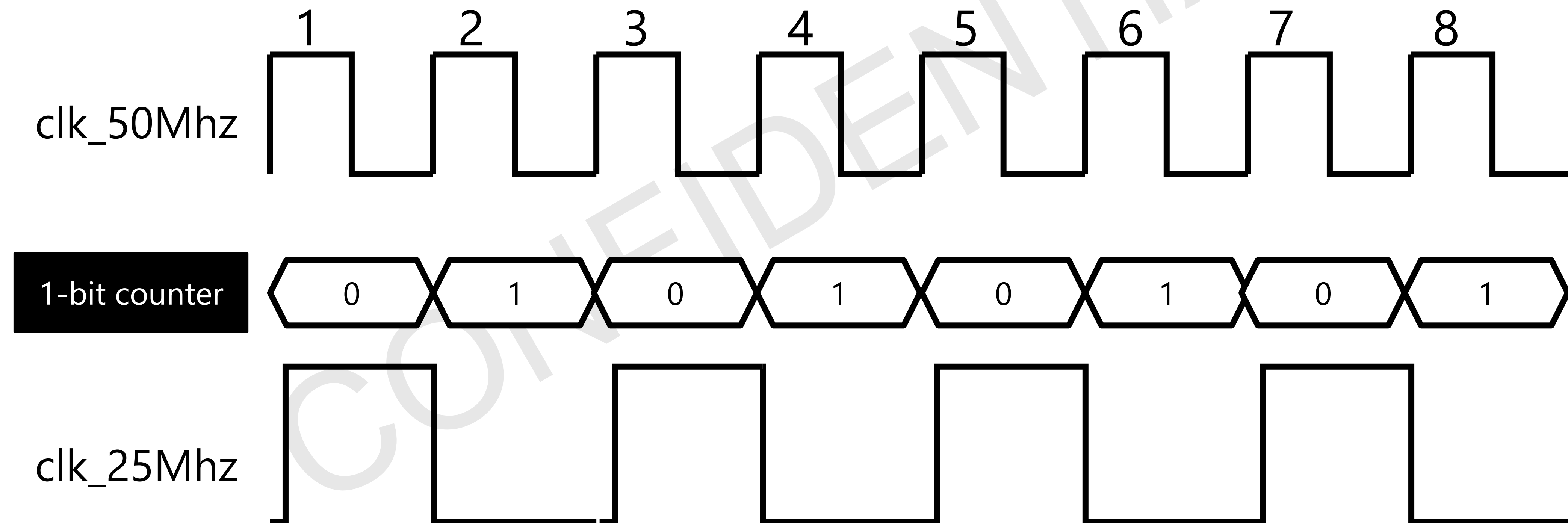A frequency divider takes a clock as input and generates a clock with a lower frequency. Typically, when done via a counter:




Frequency divider

We can calculate the output frequency via:

$$f_{out} = f_{in} / N$$

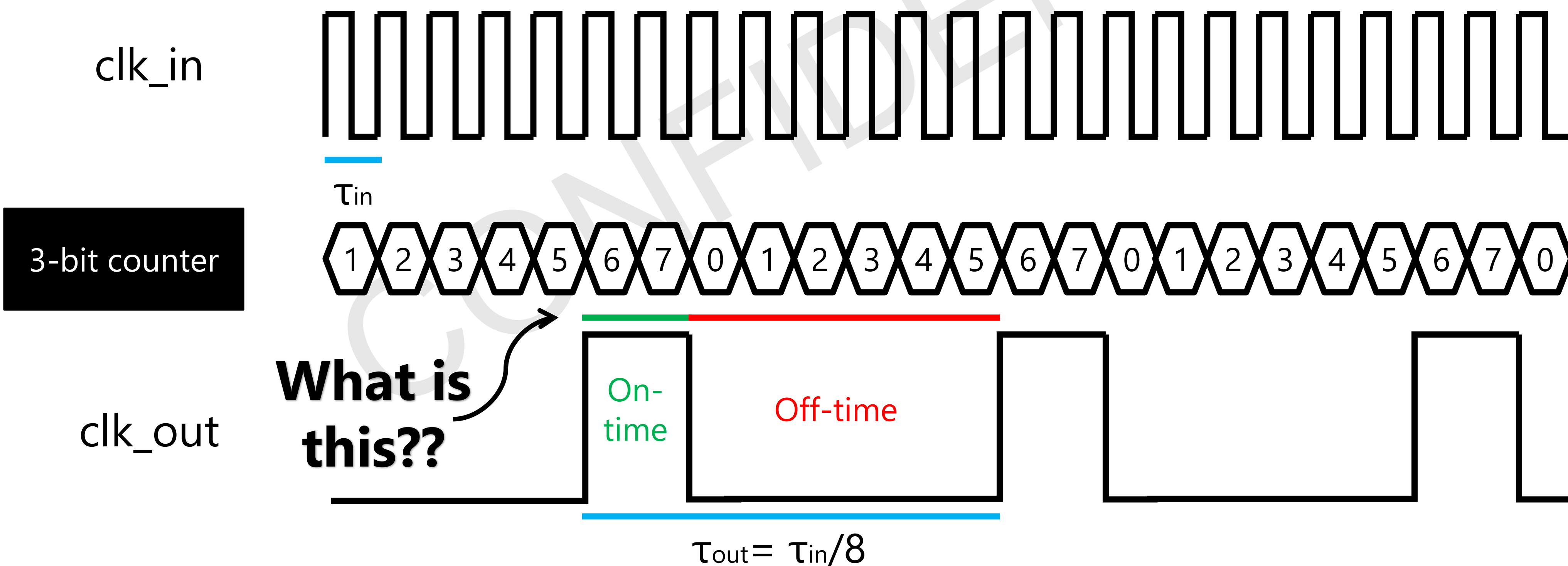Where N-1 is the max count value (e.g. for a count from 0 to 7 N=8).




Frequency divider

We can calculate the output frequency via:

$$f_{out} = f_{in} / N$$

$$\text{Duty cycle} = t_{on} / \tau_{out} = N_{on} / N$$

Where N-1 is the max count value (e.g. for a count from 0 to 7 N=8).

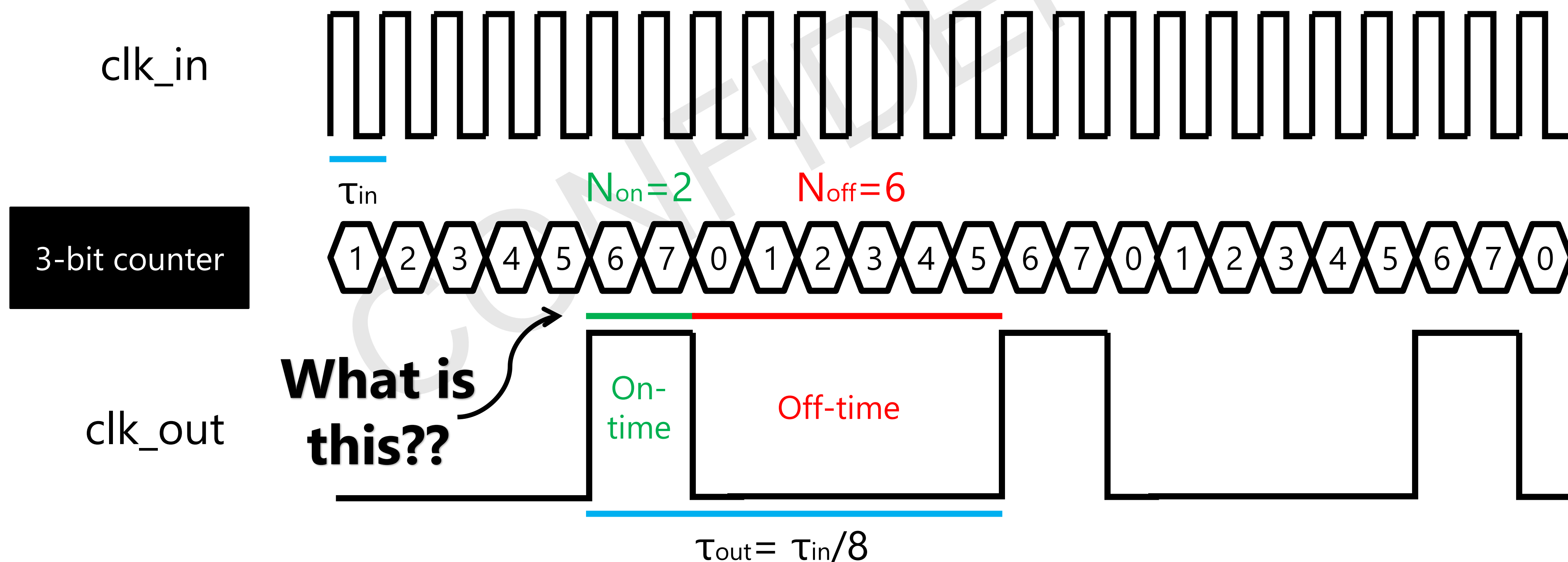

Lab 5A: Blink

Design a circuit that blinks an LED with a 1-second on / 1-second off period in a continuous loop.



CONFIDENTIAL

Lab 5B: Counter

Design a counter that increment every second. Display the count in a 7 seg display.

CONFIDENTIAL

Challenge

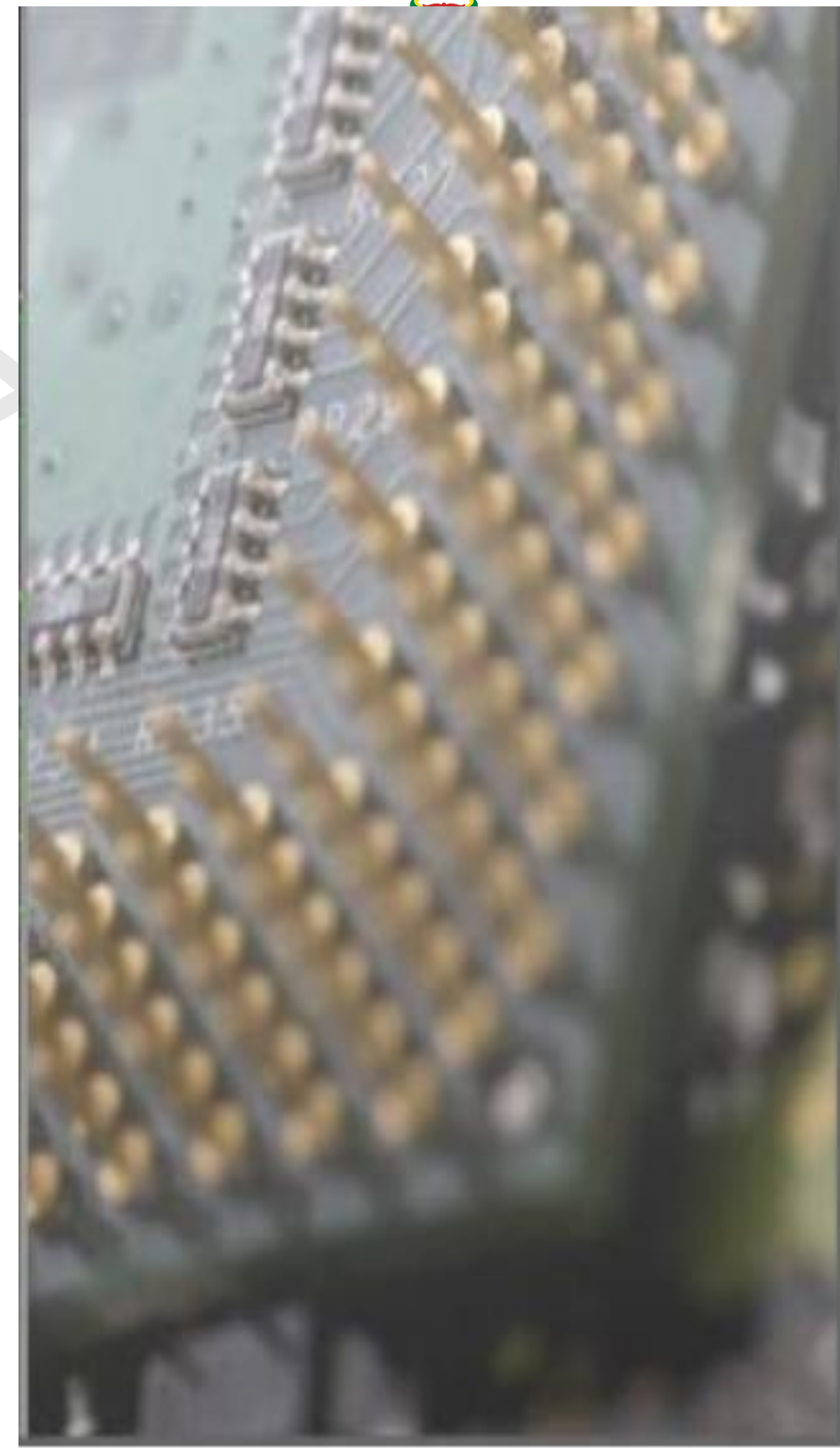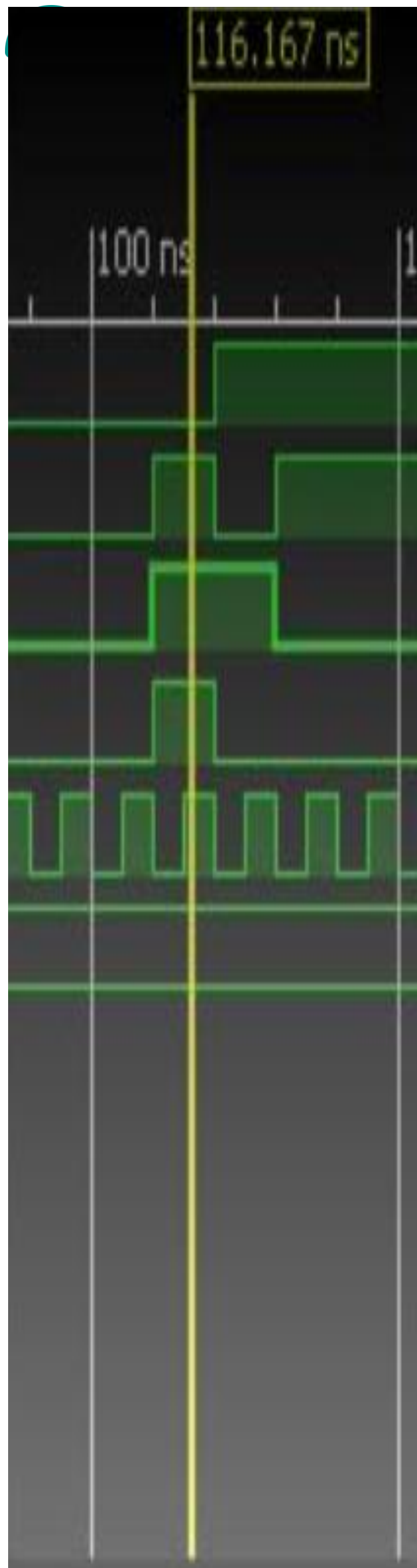

PWM

Design an 8-bits PWM (frequency at the designer consideration).

CONFIDENTIAL