

Shift register

MC. Martin González Pérez




CONFIDENTIAL

Agenda

- Shift register
- Adding features
- Car Lights


CONFIDENTIAL

Shift register

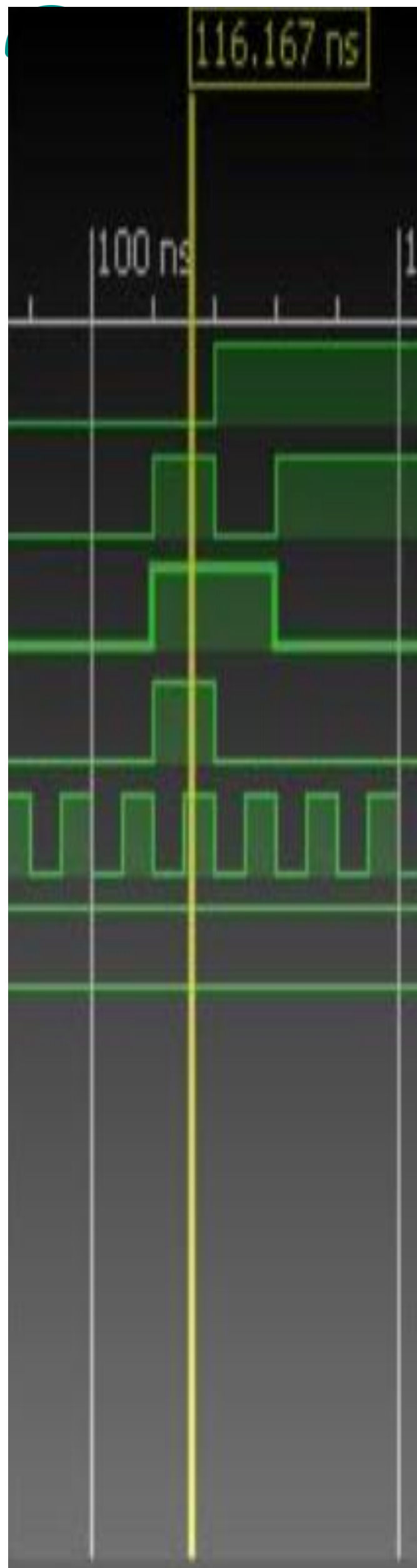

Lab 4A- Shift register

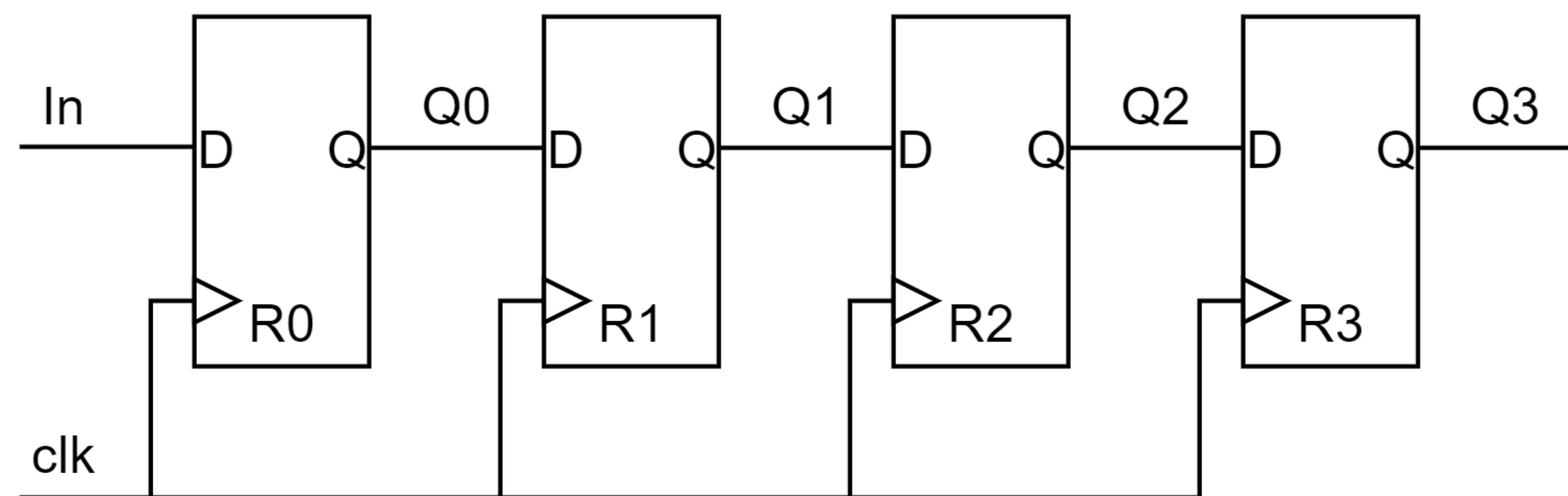Design a parametrizable shift register using Verilog.






Adding features





LAB 4B-Shift register

Design a parametrizable shift register with the next features using Verilog.

- The circuit must include an **asynchronous reset signal (arstn)**.
- The register must have an **input (in)** to allow data to be introduced into the shift register.
- The circuit must include an **enable input (shift_en)** to control the bit shifting.
- The circuit must include a **direction input (dir)** to indicate the shift direction.
 - If **dir = 1**, the shift must be to the **left**.
 - If **dir = 0**, the shift must be to the **right**.
- The circuit must include a **rotation input (rot_in)** that enables data insertion.
 - If **rot_in = 1**, the value of **in** is inserted into the shift register at the **MSb or LSb**, depending on the **dir** value.
 - If **rot_in = 0**, the bits in the register rotate:
 - The **MSb moves to the LSb** when **dir = 1**.
 - The **LSb moves to the MSb** when **dir = 0**.

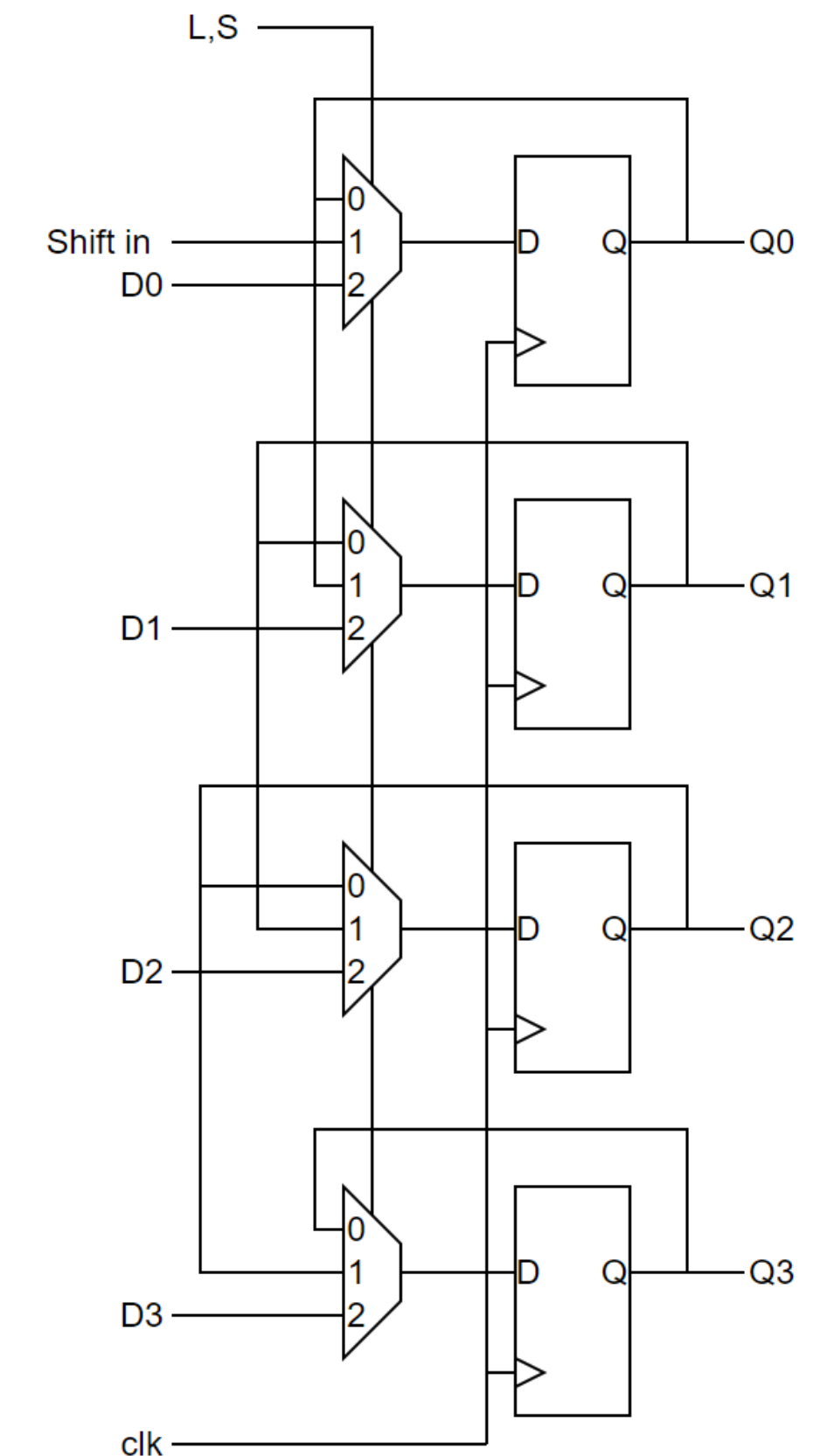

Challenge

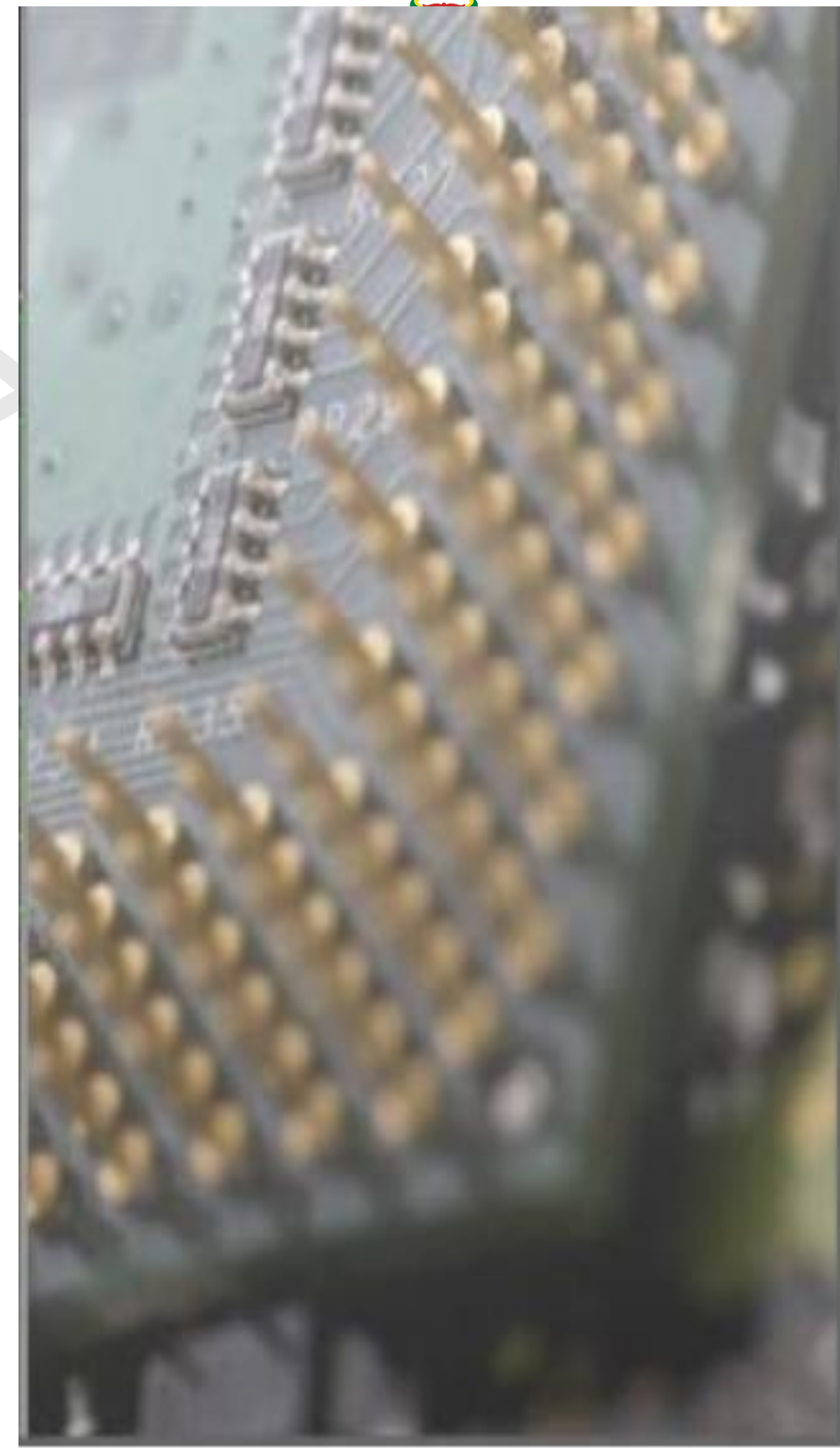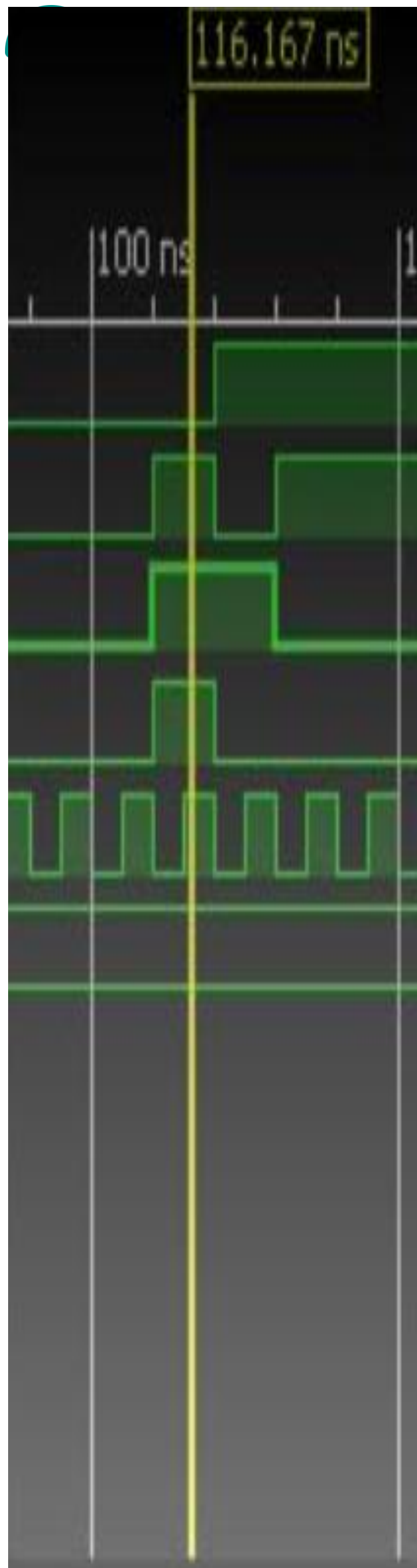

Car light

Design a circuit that perform the next light sequences.

